
Galagino CYD wiring diagram

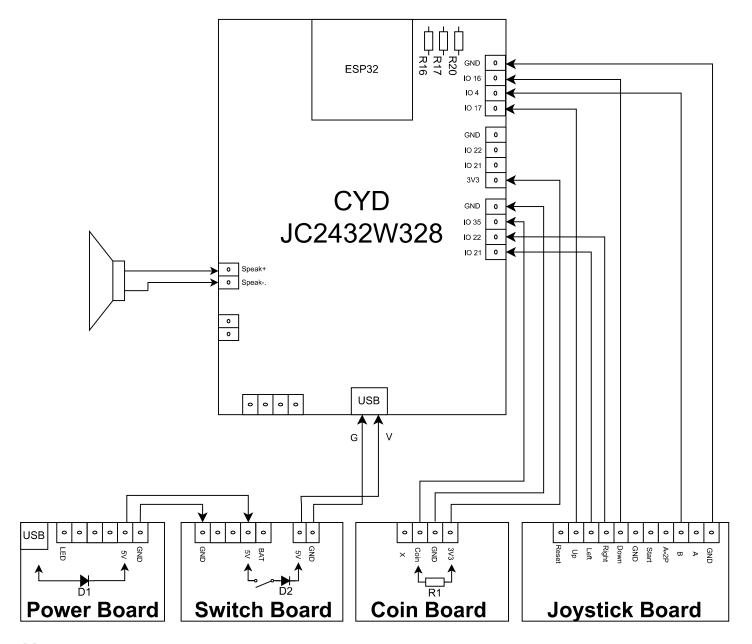

Notes:

- * R16 + R17 + R20: Remove resistors.
- * D1 + D2: Remove and bridge protection diodes. Otherwise, the voltage will be too low and ESP32 reboots.
- * R1: Add a 1kOhm pullup resistor between Coin and 3V3.
- * USB plug to CYD: I use a plug from a USB cable. Open the plug using a knife.